

Roll No. ....

Total Pages : 3

**GSE/M-21**

**1480**

PHYSICS

(Semiconductor Devices)

Paper-II

Time : Three Hours]

[Maximum Marks : 40

**Note :** Q. No. 1 is compulsory. Attempt *four* more questions selecting *one* question from each unit. All questions carry equal marks. Use of Non-programmable calculator is allowed.

**Compulsory Question**

1. (a) Discuss effect of temperature on the electrical conductivity of a semiconductor. 2
- (b) What is a load line ? How is it obtained. 2
- (c) What are positive and negative feed backs ? 2
- (d) Why Emitter follower has high input impedance ? 2


**UNIT-I**

2. (a) Describe Zener Diode. Discuss how it is used as a constant voltage regulator ? 5
- (b) Describe  $\pi$ -filter. 3

3. (a) What is a Rectifier ? Derive expressions for ripple factor of a half wave rectifier. 5
- (b) What is a P-N Junction Diode ? Explain its action forward and reverse biasing. 3

### UNIT-II

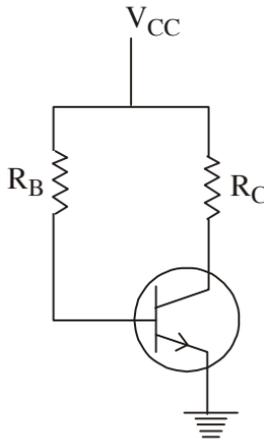4. (a) Discuss the input and output characteristics of a transistor in common base configuration and draw a circuit to obtain these characteristics. 6
- (b) Calculate the collector current and the collector to the emitter voltage in the following circuit. Take  $R_B = 300 \text{ K ohm}$ ,  $R_C = 2 \text{ K ohm}$ ,  $B = 50$ ,  $V_{CC} = 6 \text{ V}$ .



2

5. (a) Draw a circuit and explain working of NPN transistor. 4
- (b) Explain collector to Base Bias circuit. 4

### UNIT-III

6. Draw the circuit diagram of a two stage RC coupled amplifier and explain the use of different resistances and capacitances. Explain the frequency response. 8
7. (a) Draw a circuit for common emitter amplifier and explain its working. 5
- (b) How the use of negative feed back in an amplifier improves its gain stability ? 3

### UNIT-IV

8. (a) Draw a circuit for common emitter collector tuned oscillator and explain its working. 6
- (b) The tuned collector oscillator circuit used in the local oscillator of a radio receiver make use of an LC tuned circuit with  $L = 0.1 \text{ mH}$  and  $C = 400 \text{ pf}$  calculate the frequency of oscillations. 2
9. Give the construction and working of CRO. Discuss its uses. 8
-